

System components:

- main module
- 2x Flip-Flop counter \rightarrow first for 0-9, second for 0-90
- seven segment
- clk 1 sec



